

Instructions:


1. Do all of your work on this sheet.
2. **Show all of your steps** in problems for full credit.
3. **Be clear and neat** in your work. Any illegible work, or scribbling in the margins, will not be graded.
4. Place your **answers in a box**.
5. If you need more space, you may use the back of the page and write **On back** in the problem space.

1. **Multiple Guess (3 pts)** Find the answer which best fits the question and write it in the space provided.

- a. In an RC circuit the voltage \_\_\_\_\_ the current.  
 a) lags; b) leads. c) is in phase with; \_\_\_\_\_
- b. The impedance has units of \_\_\_\_\_  
 a) farads; b) ohms; c) hertz d) henries e) none of these \_\_\_\_\_
- c. According to Faraday's Law, the induced emf is a result of \_\_\_\_\_  
 a) capacitance; b) voltage; c) change in flux; d) none of these. \_\_\_\_\_

2. **Definition/Principle (4 pts)**

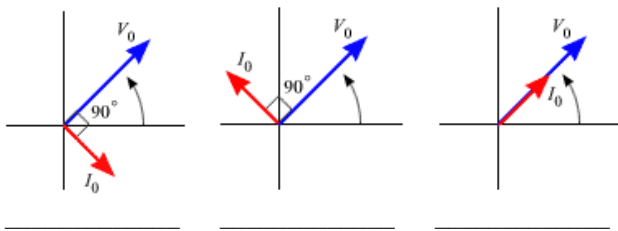- a. Indicate which phasor diagrams below are for a resistor, a capacitor, and an inductor.




- b. Give the exact expression for the self-inductance of a solenoid.

**Bonus.** What peak voltage is needed to create an rms current of 29.0 A in a circuit containing only a 5.65  $\mu\text{F}$  capacitor, when the frequency of the source is 2.60 kHz?

3. **Problems (13 pts)**

- a. On the same bar of iron are wound two coils, one with 40 loops and the other with 18. If a 20.0V alternating voltage is connected to the 40 loop coil, what will be the voltage in the 18 loop coil?

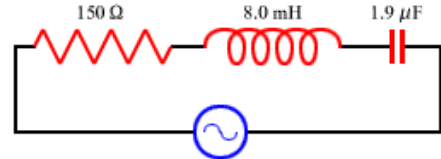- b. What is the resonant frequency of the given circuit?



- c. The mutual inductance between two coils is  $M = 6.0 \text{ mH}$ . The current in the primary coil changes at a constant rate from 2.0 A to 5.5 A in 0.020 s. What is the magnitude of the average emf induced in the secondary coil?

- d. A series LRC circuit includes a resistance of 160  $\Omega$ , an inductive reactance of 357  $\Omega$ , and a capacitive reactance of 257  $\Omega$ . If the voltage source has an rms voltage of 50.0 V, operating at 1.50 kHz. Determine the following:

i. Impedance

ii. Rms Current

iii. Phase

iv. Does the current lead, or lag, the voltage? \_\_\_\_\_