

Instructions:


1. Do all of your work on this sheet.
2. **Show all of your steps** in problems for full credit.
3. **Be clear and neat** in your work. Any illegible work, or scribbling in the margins, will not be graded.
4. Place your **answers in a box**.
5. If you need more space, you may use the back of the page and write **On back** in the problem space.

1. **Multiple Guess (3 pts)** Find the answer which best fits the question and write it in the space provided.

- a. In an RC circuit the voltage \_\_\_\_\_ the current.  
 a) lags; b) leads. c) is in phase with; a
- b. The impedance has units of \_\_\_\_\_  
 a) farads; b) ohms; c) hertz d) henries e) none of these b
- c. According to Faraday's Law, the induced emf is a result of \_\_\_\_\_  
 a) capacitance; b) voltage; c) change in flux; d) none of these. c

2. **Definition/Principle (4 pts)**

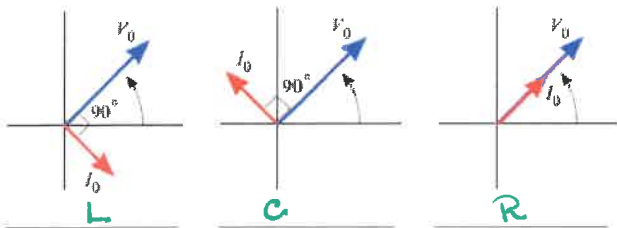a. Indicate which phasor diagrams below are for a resistor, a capacitor, and an inductor.



b. Give the exact expression for the inductive reactance in terms of the inductance and frequency.

$$X_L = 2\pi f L$$

**Bonus.** A 25cm x 15cm coil rotates in a 1.60 T field at 75 Hz. If the generated emf has peak value of 56.59 V, then how many loops are in the coil?


$$\begin{aligned} \mathcal{E}_0 &= NBA\omega \\ N &= \frac{56.59}{1.6(0.25)(0.15)2\pi(75)} = 2 \end{aligned}$$

3. **Problems (13 pts)**

a. On the same bar of iron are wound two coils, one with 40 loops and the other with 18. If a 20.0V alternating voltage is connected to the 40 loop coil, what will be the voltage in the 18 loop coil?

$$V_s = \frac{N_s}{N_p} V_p = \frac{18}{40} (20) = 9 \text{ V}$$

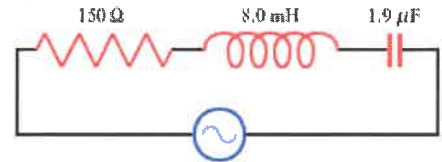b. What is the resonant frequency of the given circuit?



$$\begin{aligned} X_L &= X_C \\ f_0 &= \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{1.9 \times 10^{-6} (8 \times 10^{-3})}} \\ &= \frac{1}{2\pi\sqrt{1.52 \times 10^{-8}}} = 1290 \text{ Hz} \end{aligned}$$

c. What peak voltage is needed to create an rms current of 29.0 A in a circuit containing only a 5.65 microF capacitor, when the frequency of the source is 2.60 kHz?

$$\begin{aligned} V_{rms} &= I_{rms} X_C = \frac{29}{2\pi(2.6 \times 10^3)(5.65 \times 10^{-6})} \\ &= .314 \times 10^3 = 314 \text{ V} \\ V_0 &= 314\sqrt{2} = 444 \text{ V} \end{aligned}$$

d. A series LRC circuit includes a resistance of 160 Ohm, an inductive reactance of 357 Ohm, and a capacitive reactance of 257 Ohm. If the voltage source has an rms voltage of 50.0 V, operating at 1.50 kHz. Determine the following:

i. Impedance

$$Z = \sqrt{160^2 + 100^2} = 189 \Omega$$

ii. Rms Current

$$I_{rms} = \frac{V_{rms}}{Z} = 0.26 \text{ A}$$

iii. Phase

$$\tan \phi = \frac{100}{160} \Rightarrow \phi = 32^\circ$$

iv. Does the current lead, or lag, the voltage? lag